



[Answer all the questions]

2. a) **Implement** the following Boolean function using a multiplexer (MUX). [05]

Here, $D = (X_1X_2X_3+5) \bmod 7$ where $X_1X_2X_3$ denotes the last 3 digits of your ID.

- $$F1 = \sum(N, N + 1, N + 3, N + 4, N + 7, N + 8, N + 10)$$

3. a) Analyze R-S flip-flop to find out the limitations and **characterize** a solution to overcome the limitation. [05]

- [illegible]

4. a) **Explain** briefly the implementation of BCD ripple counter with J-K flip flop. [05]
- b) Consider the following operating mode and **design** a shift register using MUX to perform all the operations. [05]

S0	S1	Operating Mode
0	0	Locked
1	0	Shift-Right
0	1	Shift-Left
1	1	Parallel Loading